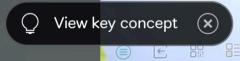


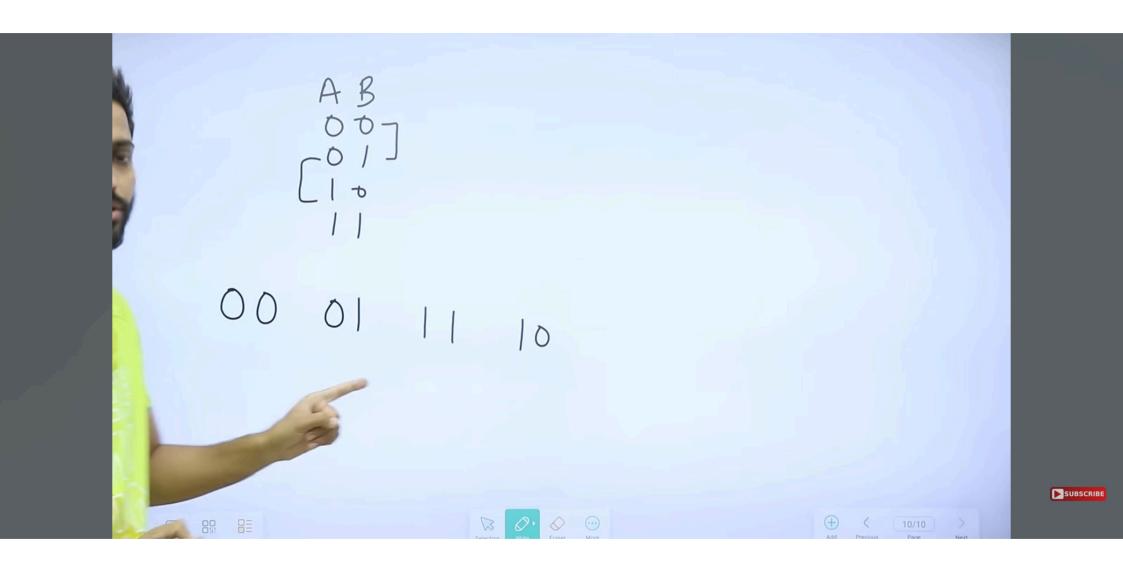
- K Map is a graphical representation used for simplifying the Boolean expressions.
- For a Boolean expression consisting of n-variables, number of cells required in K Map = 2ⁿ cells.
- K Map is based on Grey code(Unit distance code).
- K Map is based on three types of Input values(0, 1, don't care)

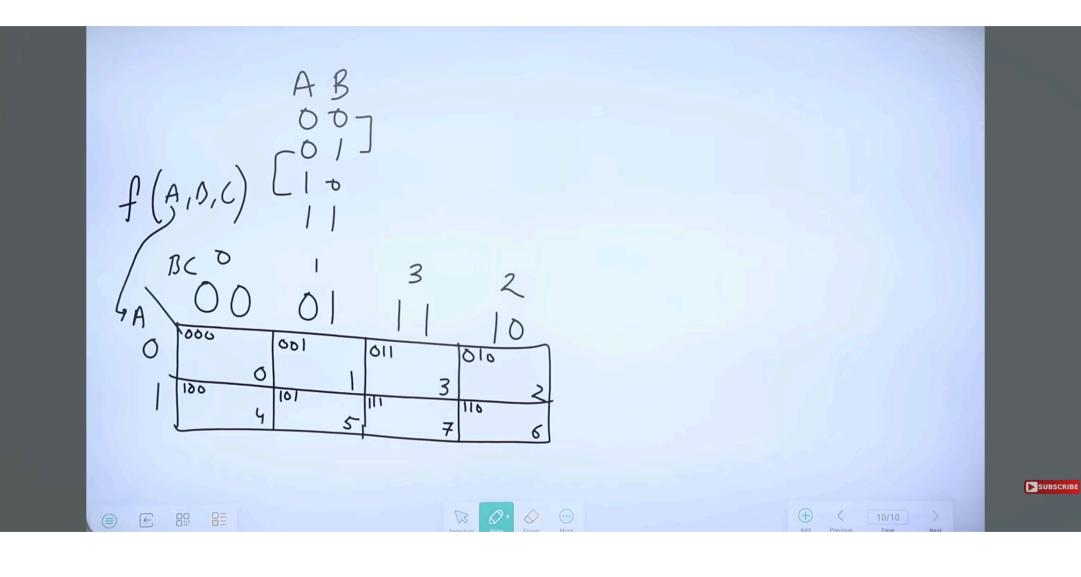


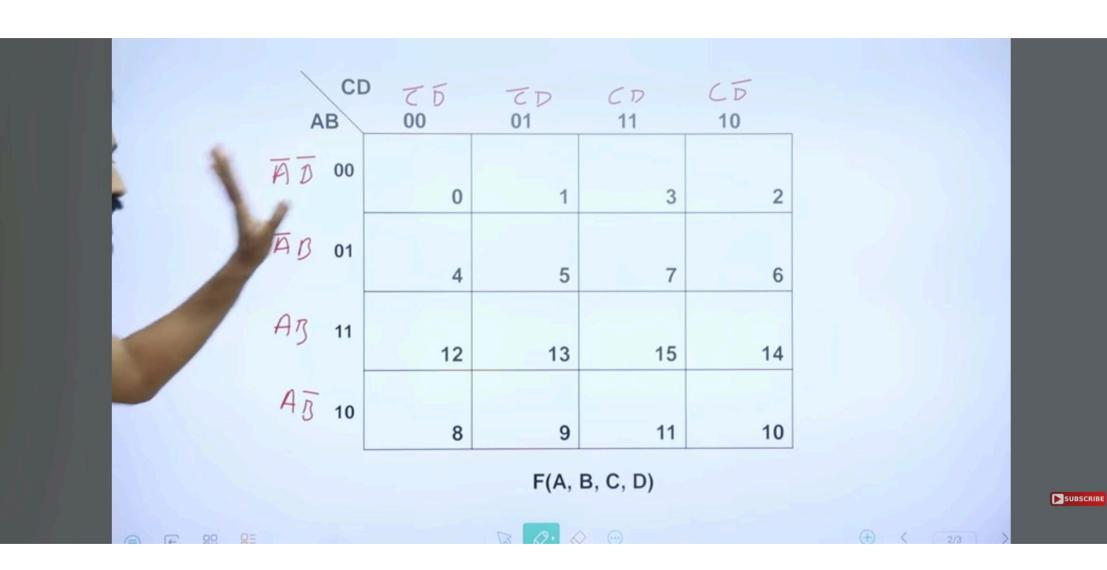




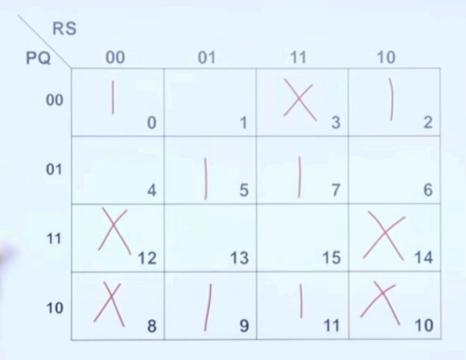






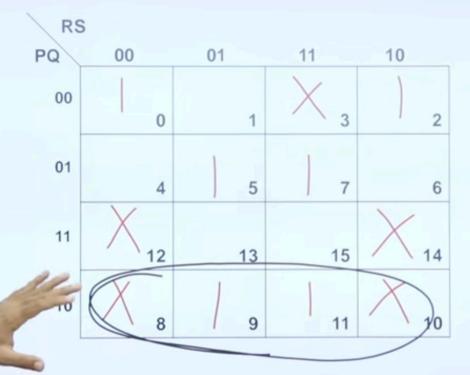




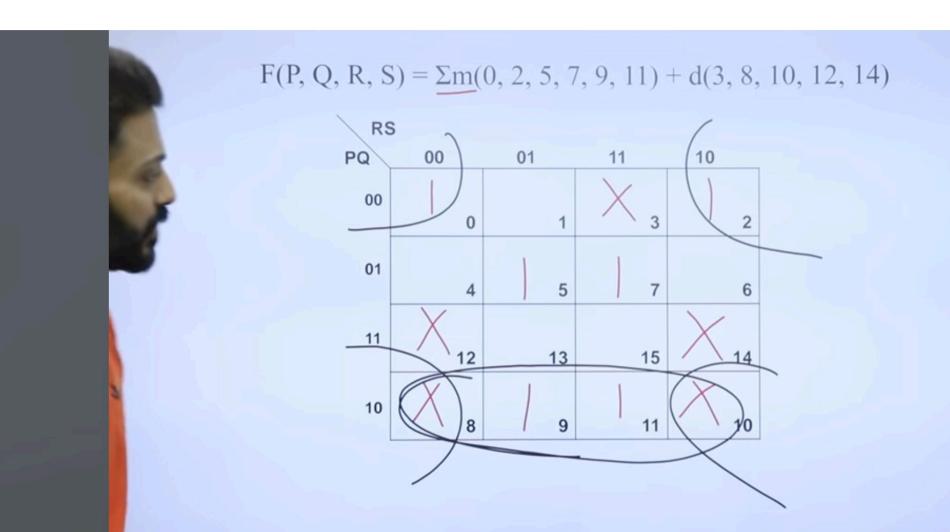




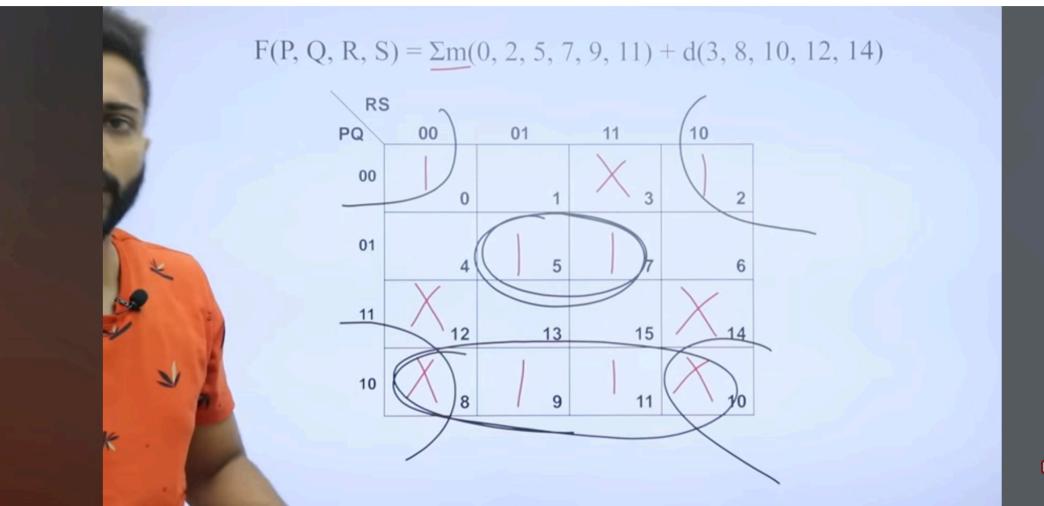




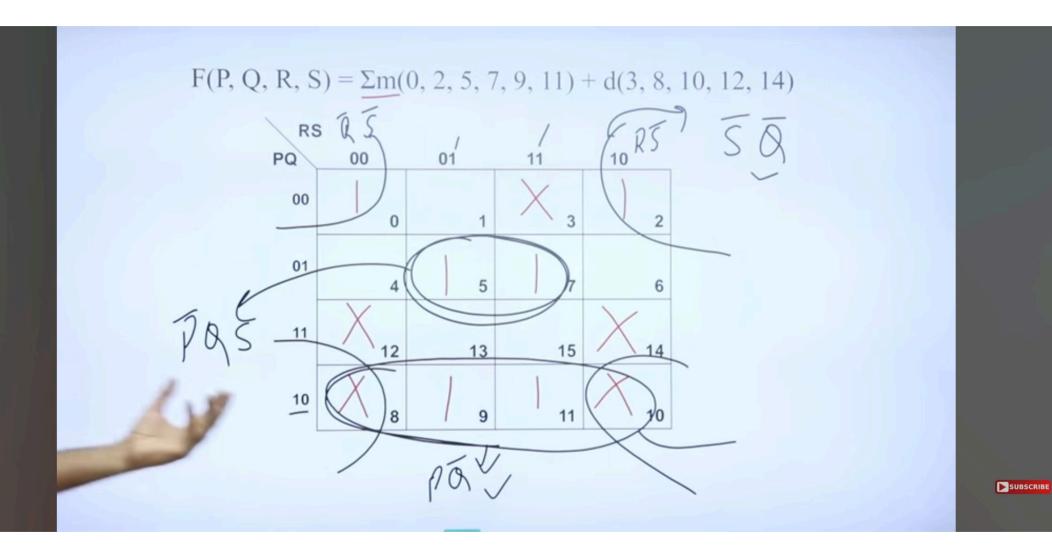












Two possibilities

Minterms Maxterms

Σm(1,2,3,5,6,7,10) F(A,B,C,D) = AB+ ABC + CD πM(1,2,4,5)

Boolean Expression will be given in question given in question

$$F(A,B,C,D) = AB + ABC + CD$$

Title

Q1. Simplify boolean function using K-map in sop and pos forms and implement with gates.

$$f(A,B,C) = \sum_{m} (0,2,3,4,5,6)$$

Note
$$\rightarrow \mathbb{Z}m()$$
 Minterms $\rightarrow SOP \rightarrow when F=1$
So put 1' in kMap

TTM - Mautorma - DOC - Illa T-A

< Title

una impierient with gates

$$f(A,B,C) = \sum_{m} (0,2,3,4,5,6)$$

Note
$$\rightarrow \text{Zm}()$$
 Minterms $\rightarrow \text{SOP} \rightarrow \text{when } F=1$
So put 1' in kMap

TTM
$$\longrightarrow$$
 Maxterms \longrightarrow POS \longrightarrow When $F=0$
So put \bigcirc in kMap

