

# **DIGITAL LOGIC CIRCUITS**

---

**Logic Gates**

**Boolean Algebra**

**Map Specification**

**Combinational Circuits**

**Flip-Flops**

**Sequential Circuits**

**Memory Components**


**Integrated Circuits**

# LOGIC GATES

## Digital Computers

- Imply that the computer deals with digital information, i.e., it deals with the information that is represented by binary digits
- Why *BINARY* ? instead of Decimal or other number system ?

\* Consider electronic signal

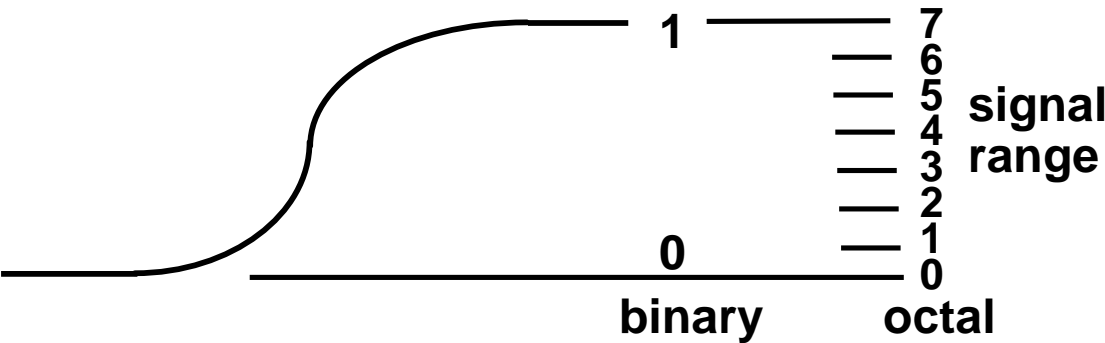


\* Consider the calculation cost - Add

	0	1
0	0	1
1	1	10

	0	1	2	3	4	5	6	7	8	9
0	0	1	2	3	4	5	6	7	8	9
1	1	2	3	4	5	6	7	8	9	10
2	2	3	4	5	6	7	8	9	10	11
3	3	4	5	6	7	8	9	10	11	12
4	4	5	6	7	8	9	10	11	12	13
5	5	6	7	8	9	10	11	12	13	14
6	6	7	8	9	10	11	12	13	14	15
7	7	8	9	10	11	12	13	14	15	16
8	8	9	10	11	12	13	14	15	16	17
9	9	10	11	12	13	14	15	16	17	18

## BASIC LOGIC BLOCK - GATE -

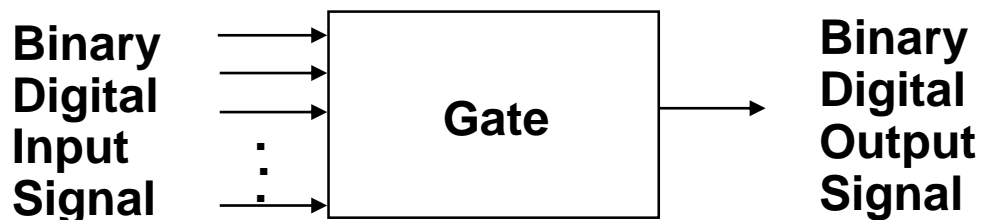

### Types of Basic Logic Blocks

- **Combinational Logic Block**

Logic Blocks whose output logic value depends only on the input logic values









- **Sequential Logic Block**

Logic Blocks whose output logic value depends on the input values and the state (stored information) of the blocks

### Functions of Gates can be described by

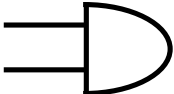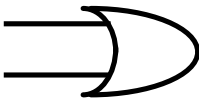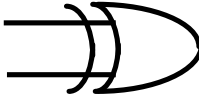- **Truth Table**
- **Boolean Function**
- **Karnaugh Map**

COMBINATIONAL GATES

Name	Symbol	Function	Truth Table															
AND	<div><div>A</div><div>B</div></div> X	$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR	<div><div>A</div><div>B</div></div> X	$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I	<div><div>A</div></div> X	$X = A'$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer	<div><div>A</div></div> X	$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND	<div><div>A</div><div>B</div></div> X	$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR	<div><div>A</div><div>B</div></div> X	$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR	<div><div>A</div><div>B</div></div> X	$X = A \oplus B$ or $X = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR Exclusive NOR or Equivalence	<div><div>A</div><div>B</div></div> X	$X = (A \oplus B)'$ or $X = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

# BOOLEAN ALGEBRA

## Boolean Algebra


- \* Algebra with Binary(Boolean) Variable and Logic Operations
- \* Boolean Algebra is useful in Analysis and Synthesis of Digital Logic Circuits
  - Input and Output signals can be represented by Boolean Variables, and
  - Function of the Digital Logic Circuits can be represented by Logic Operations, i.e., Boolean Function(s)
  - From a Boolean function, a logic diagram can be constructed using AND, OR, and I

## Truth Table


- \* The most elementary specification of the function of a Digital Logic Circuit is the Truth Table
  - Table that describes the Output Values for all the combinations of the Input Values, called *MINTERMS*
  - n input variables  $\rightarrow 2^n$  minterms

# LOGIC CIRCUIT DESIGN

Truth Table

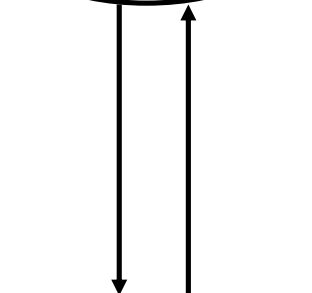


Boolean Function

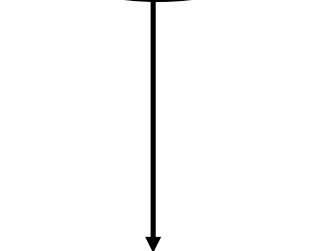

Logic Diagram

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$F = x + y'z$

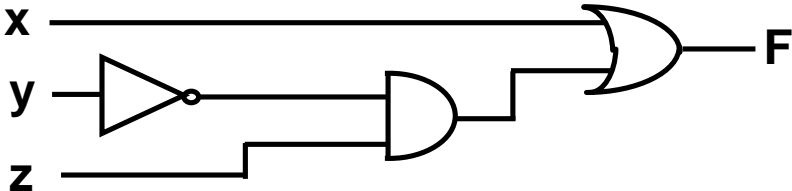

# BASIC IDENTITIES OF BOOLEAN ALGEBRA

$$[1] \quad x + 0 = x$$

$$[3] \quad x + 1 = 1$$

$$[5] \quad x + x = x$$

$$[7] \quad x + x' = 1$$

$$[9] \quad x + y = y + x$$

$$[11] \quad x + (y + z) = (x + y) + z$$

$$[13] \quad x(y + z) = xy + xz$$

$$[15] \quad (x + y)' = x'y'$$

$$[17] \quad (x')' = x$$

$$[2] \quad x \cdot 0 = 0$$

$$[4] \quad x \cdot 1 = x$$

$$[6] \quad x \cdot x = x$$

$$[8] \quad x \cdot x' = 0$$

$$[10] \quad xy = yx$$

$$[12] \quad x(yz) = (xy)z$$

$$[14] \quad x + yz = (x + y)(x + z)$$

$$[16] \quad (xy)' = x' + y'$$

[15] and [16] : De Morgan's Theorem

## Usefulness of this Table



- Simplification of the Boolean function
  - Derivation of equivalent Boolean functions to obtain logic diagrams utilizing different logic gates
    - Ordinarily ANDs, ORs, and Inverters
    - But a certain different form of Boolean function may be convenient to obtain circuits with NANDs or NORs
- Applications of De Morgans Theorem

$$x'y' = (x + y)'$$

I, AND → NOR

$$x' + y' = (xy)'$$

I, OR → NAND

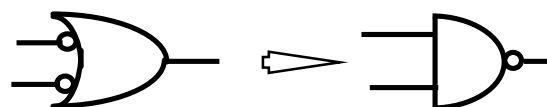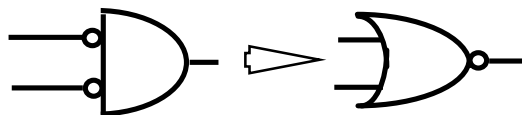

EQUIVALENT CIRCUITS

Many different logic diagrams are possible for a given Function


$$F = ABC + ABC' + A'C$$
$$= AB(C + C') + A'C$$
$$= AB \cdot 1 + A'C$$
$$= AB + A'C$$

..... (1)

[13] ..... (2)

[7]

[4] ..... (3)

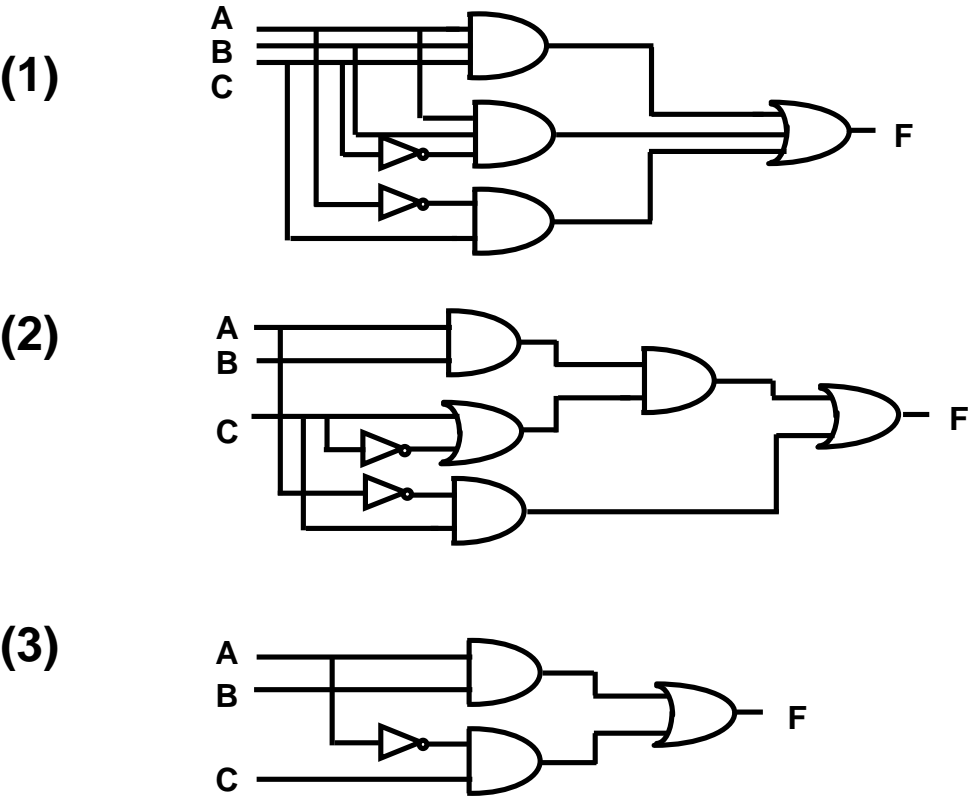



## COMPLEMENT OF FUNCTIONS

A Boolean function of a digital logic circuit is represented by only using logical variables and AND, OR, and Invert operators.

→ Complement of a Boolean function

- Replace all the variables and subexpressions in the parentheses appearing in the function expression with their respective complements

$$A, B, \dots, Z, a, b, \dots, z \Rightarrow A', B', \dots, Z', a', b', \dots, z'$$
$$(p + q) \Rightarrow (p + q)'$$

- Replace all the operators with their respective complementary operators


$$\text{AND} \Rightarrow \text{OR}$$
$$\text{OR} \Rightarrow \text{AND}$$

- Basically, extensive applications of the De Morgan's theorem


$$(x_1 + x_2 + \dots + x_n)' \Rightarrow x_1' x_2' \dots x_n'$$

$$(x_1 x_2 \dots x_n)' \Rightarrow x_1' + x_2' + \dots + x_n'$$

# SIMPLIFICATION

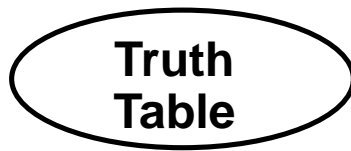

Unique

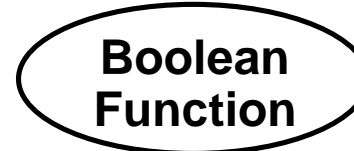

Many different expressions exist

## Simplification from Boolean function

- Finding an equivalent expression that is least expensive to implement
- For a simple function, it is possible to obtain a simple expression for low cost implementation
- But, with complex functions, it is a very difficult task

Karnaugh Map (K-map) is a simple procedure for simplifying Boolean expressions.

