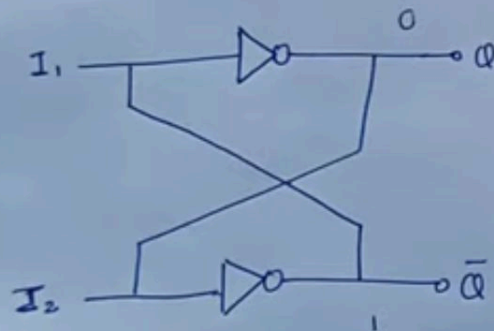


Latch v/s Flipflop




Latches

- Latches are building blocks of sequential circuits.
- Built from logic gates
- without clock



Flip Flops

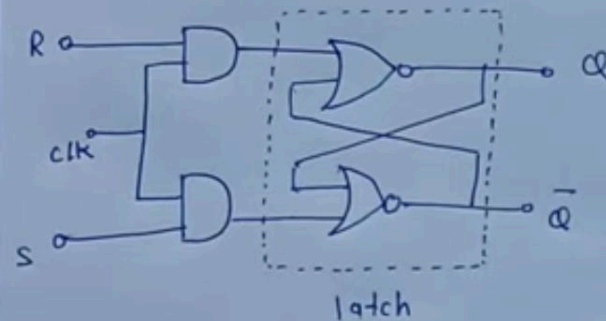
- Also sequential circuits. used to store one bit binary no. (logic 1 and 0).
- Built from latches.
- with clock.
- (JK, SR, D, T)






Latches

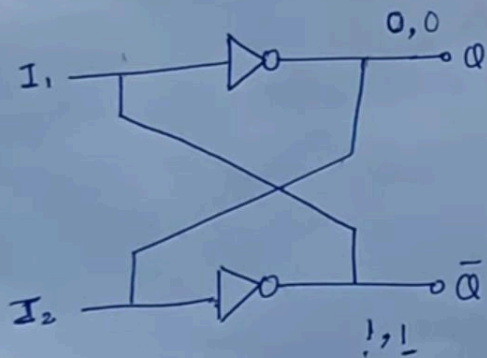- Latches are building blocks of sequential circuits.
- Built from logic gates
- without clock



Flip Flops

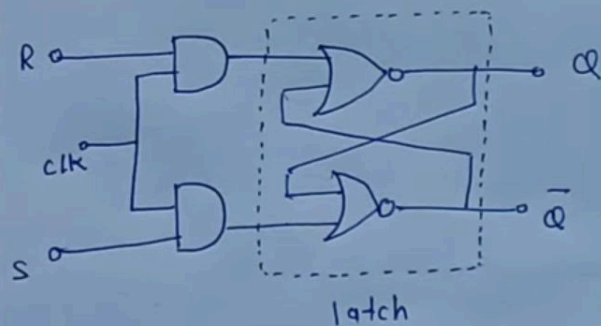- Also sequential circuits. Used to store one bit binary no. (logic 1 and 0).
- Built from latches.
- with clock.
- (JK, SR, D, T)





Latches


- Latches are building blocks of sequential circuits.
- Built from logic
- without clock

I₁




Flip Flops

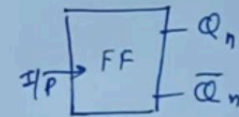- Also sequential circuits. Used to store one bit binary no. (logic 1 and 0).
- Built from latches.
- with clock.
(JK, SR, D, T)




$Q_1, Q_2,$

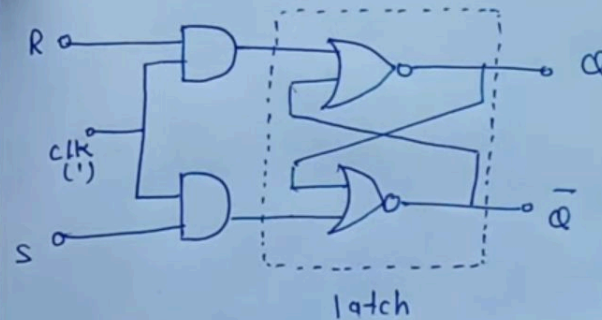

Flip-Flop




Clock Signal

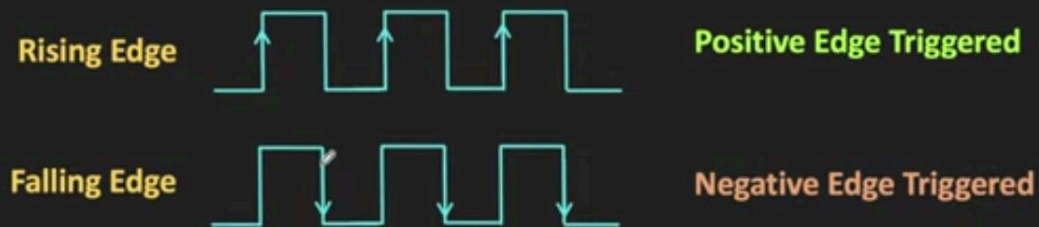

Flip-Flop



Positive Edge Triggered Flip-Flop

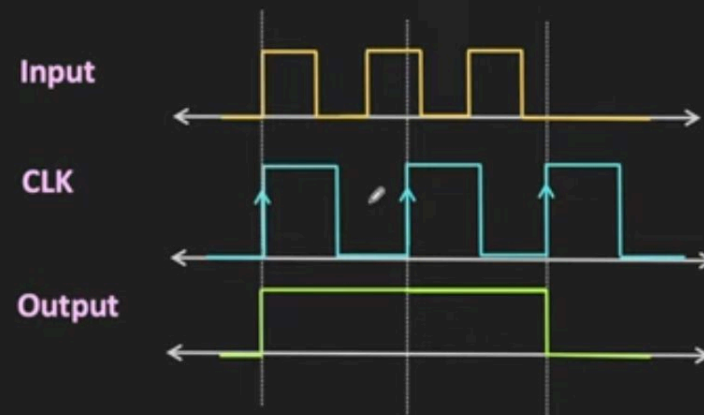


ALL ABOUT ELECTRONICS



Flip-Flop



Negative Edge Triggered Flip-Flop

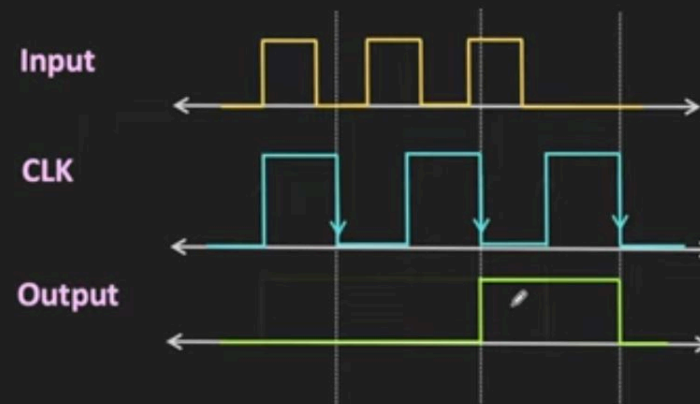

ALL ABOUT ELECTRONICS




Summary of All Flipflops

Summary of Flip-Flops

Logic diagram


S-R F/F

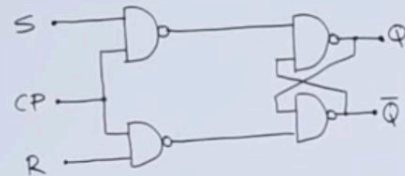


D F/F



J-K F/F

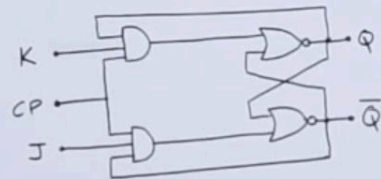

T F/F

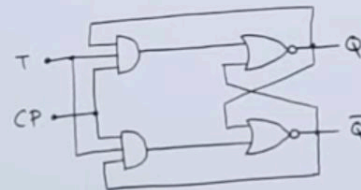

Characteristic Table

S	R	$Q(t+1)$
0	0	$Q(t)$ No Change
0	1	0 Reset
1	0	1 Set
1	1	? Indeterminate

D	$Q(t+1)$
0	0
1	1

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

Excitation Table

$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0



Summary of Flip-Flops

Logic diagram

S-R F/F

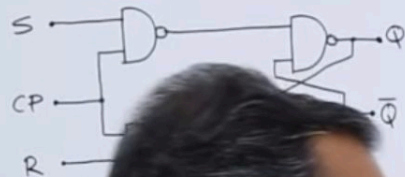

D F/F



J-K F/F



Characteristic Table

S	R	$Q(t+1)$
0	0	$Q(t)$ No Change
0	1	0 Reset
1	0	1 Set
1	1	? Indeterminate

D	$Q(t+1)$
0	0
1	1

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

Excitation Table

$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

SR to JK flipflop



SR \rightarrow JK
Given Derived
Mai MSD
Excitation Character.



J	K	Q_n	Q_{n+1}	S	R
0	0	0	0		
0	0	1	1		
0	1	0	0		
0	1	1	0		
1	0	0	1		
1	0	1	1		
1	1	0	1		
1	1	1	0		

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0		
0	0	1	1		
0	1	0	0		
0	1	1	0		
1	0	0	1		
	0	1	1		
1	1	0	1		
1	1	1	0		

Excitation


Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0



J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

Excitation


Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

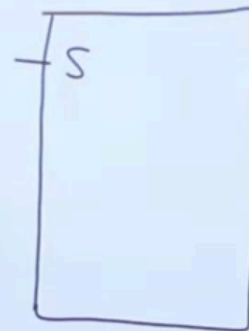

J	K	Q_{n+1}	S	R
0	0	0	0	X
0	0	1	X	0
0	1	0	0	X
0	1	1	0	1
1	0	0	1	0
1	0	1	X	0
1	1	0	1	0
1	1	1	0	0

J —

\bar{K}


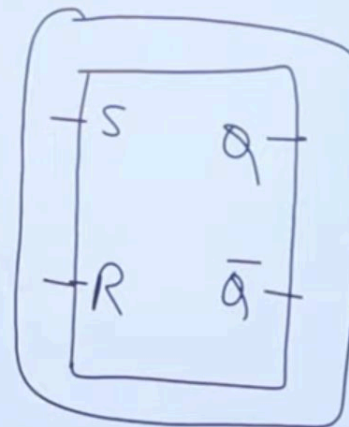


Excitation

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0



J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

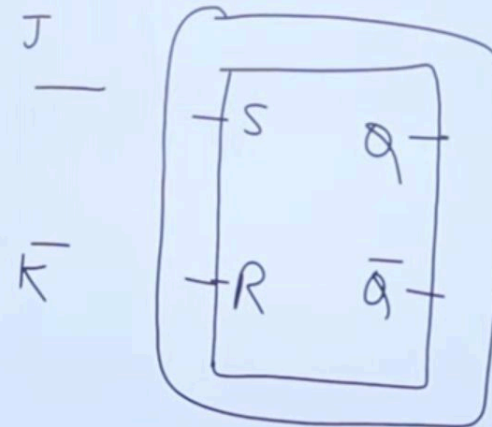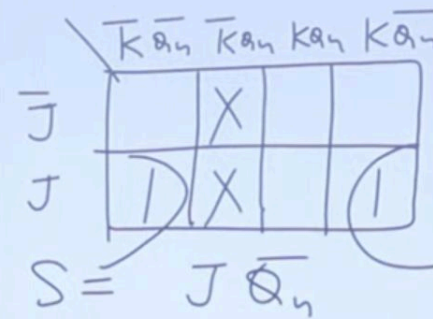


Excitation

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0




J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

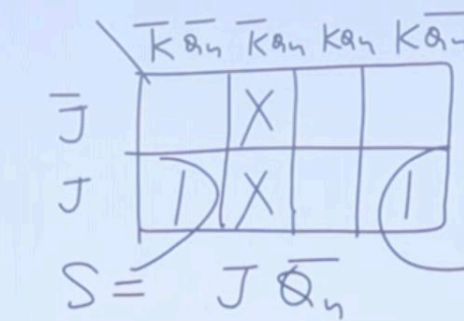


Excitation

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

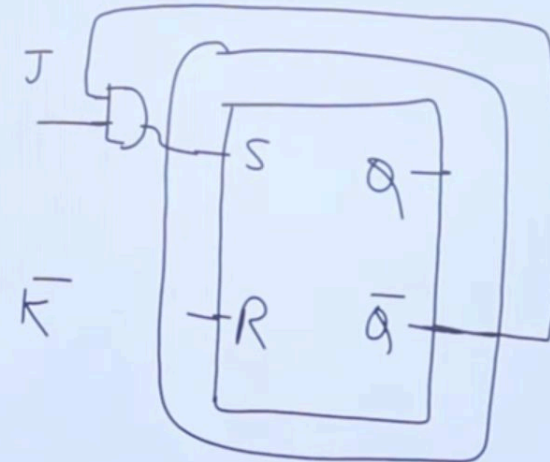

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

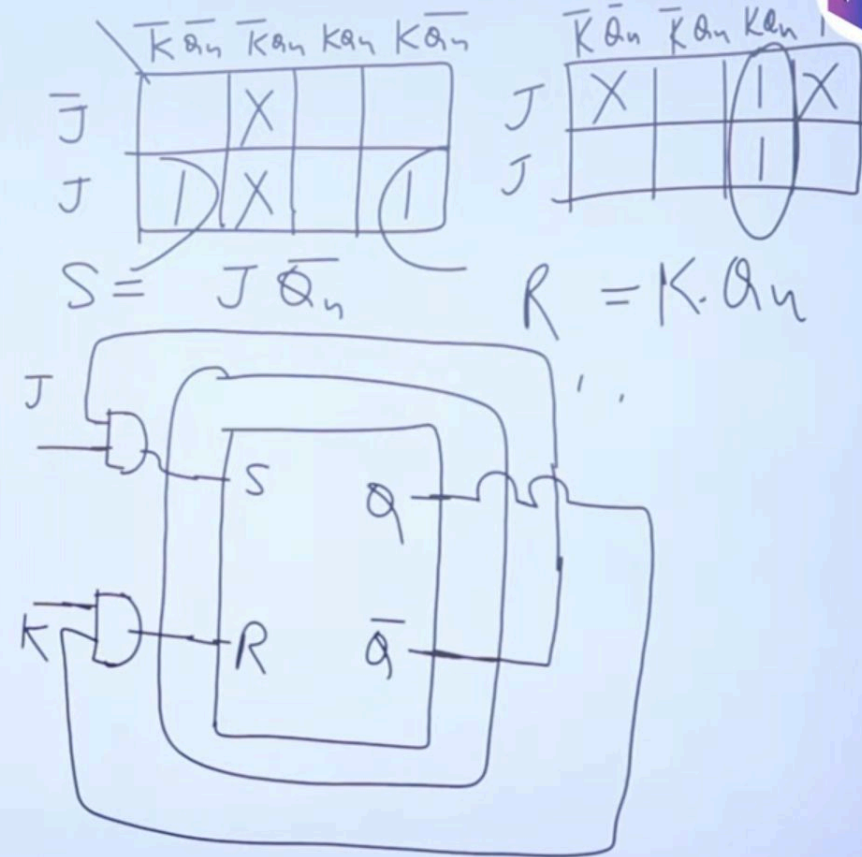

T flipflop to JK

T to JK
given Target
↓ ↓
Ex. Char.

T to JK
 given Target
 ↓ ↓
 Ex. Char.

J	K	Q_n	Q_{n+1}^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

T to JK
 given Target
 ↓ Char.
 Ex.


J	K	Q_n	Q_{n+1}^+	T
0	0	0	0	0
0	0	1	1	0
0	0	0	0	0
0	0	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

0	0	0
0	1	1
1	0	1
1	1	0

T to JK
 given
 ↓
 Ex.
 Target
 ↓
 Char.

J	K	Q_n	Q_{n+1}	T
0	0	0	0	0
0	0	1	1	0

3	0	1	1	0	✓
4	1	0	0	1	✓
5	1	0	1	0	✓
6	1	1	0	1	✓
7	1	1	0	1	✓

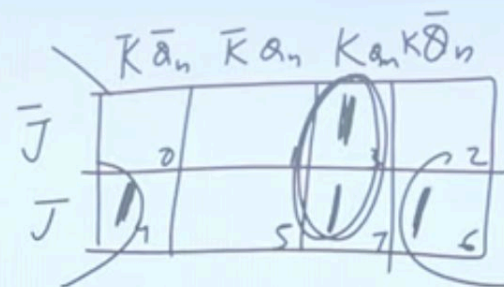


$$T = KQ_n + J\bar{Q}_n$$


0	0	0
0	1	1
1	0	1
1	1	0

T to JK
 given Target
 ↓ Char.
 Ex.

K	Q_n	Q_{n+1}	T
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1
0	0	1	1
0	1	1	1

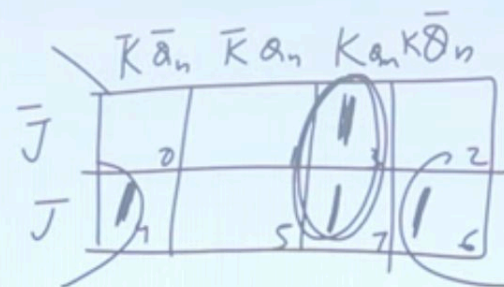

$$T = KQ_n + J\bar{Q}_n$$

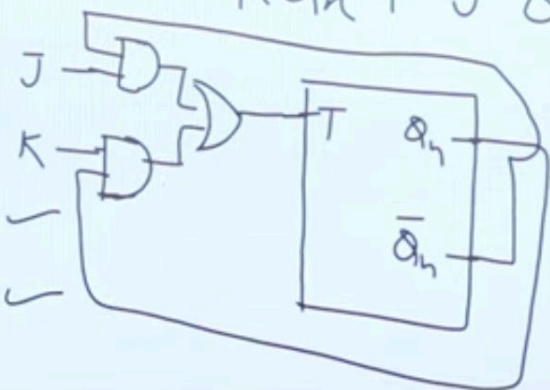

0	0	0
0	1	1
1	0	1
1	1	0